

CHAPTER 3

LOGIC CIRCUITS

Unit Objectives:


- Understand the significance of logic gates.
- Explain the rules and usage of boolean Algebra.
- Discuss the process of implementation of Boolean Algebra.
- Explain the significance of function simplification and Karnaugh maps.

LOGIC CIRCUITS

- Are electronic devices used in computers to perform logic operations on 1 or more input signals.
- Inputs and outputs to digital computers are in one of the 2 possible states / Voltage levels which are represented by 0's or 1's
- If the higher voltage is associated with 1 and lower voltage with a 0, the circuit is said to be based upon **positive logic**.
- If the lower voltage is associated with a 1 and higher voltage with 0, the circuit is said to be based on **negative logic**.

LOGIC CIRCUITS

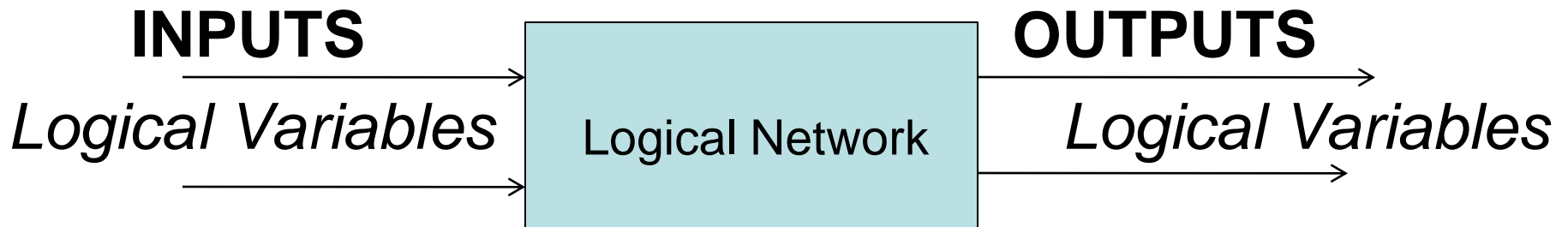- Any variable that can take on two states e.g. (0/1, True/false; on/off) is called **a logical variable**.
- A circuit whose inputs and outputs are described by logical variables is called a **logical network**.



Logical Networks

There are two types of logical networks:

- **Combinatorial networks:** Their outputs depend on the current inputs.
- **Sequential Networks:** Their outputs depend on both the current state of the network as well as the inputs


Logic Gates

- **A combinatorial circuit with only one output** is called a **logic gate**. They accept logical values at their inputs and they produce corresponding logical values at their outputs.
- It performs a logical operation on one or more binary inputs and produces a single binary output.
- **A table listing all the outputs for the various inputs** is called a **truth table**.
- All combinatorial circuits can be constructed from the 7 most common logic gates.

Logic Gates

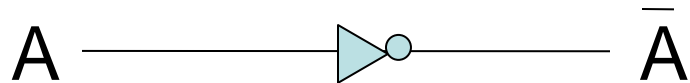
1. The inverter(NOT) Gate:

When the input is 1 the output is 0 and vice versa.



A	\bar{A}
0	1
1	0

2. The AND Gate:

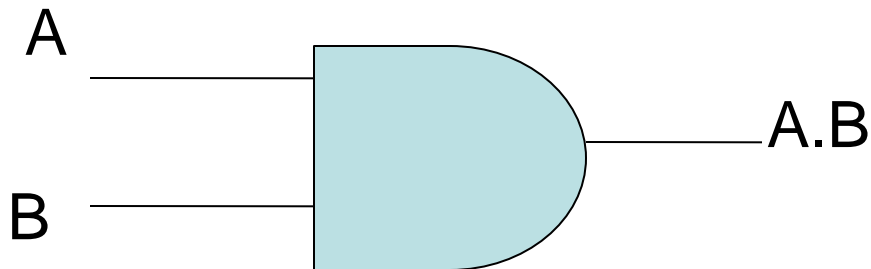


Input		Output
A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

The output is 1 if all the inputs are 1's

Logic Gates

3. The OR Gate:

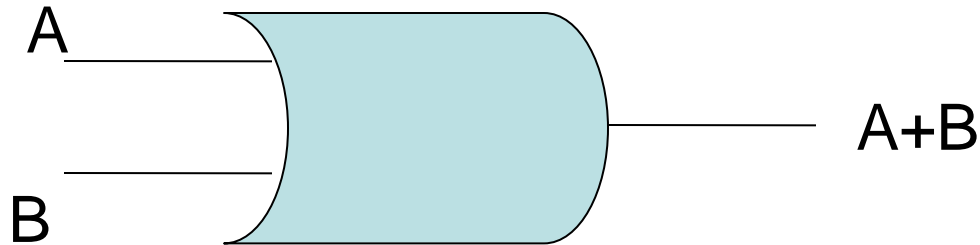


A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

- **The output is 0 if all the inputs are 0's.**
- If an inverter is combined with another logic gate, the presence of the inverter is indicated by placing a small circle at the affected input or output.

Logic Gates


4. The NAND (NOT AND) Gate

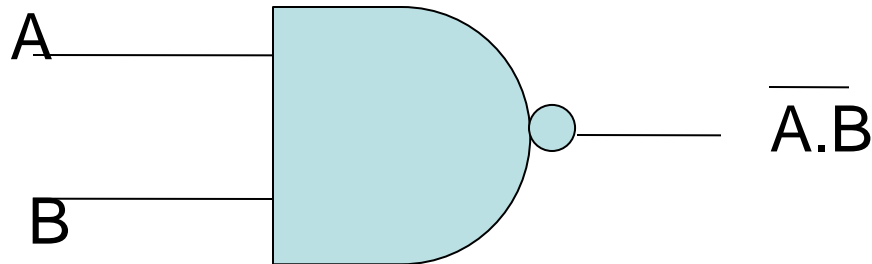

A	B	$\overline{A.B}$
0	0	1
0	1	1
1	0	1
1	1	0

The output is 0 if all the inputs are 1's.

5. The NOR (NOT OR) Gate

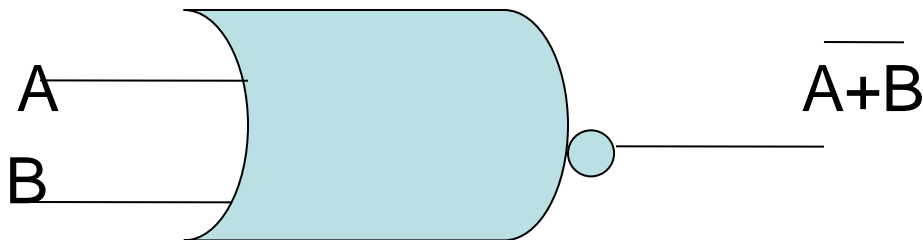


A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

The output is 1 if all the inputs are 0's.

LOGIC GATES


6. The EXCLUSIVE OR Gate

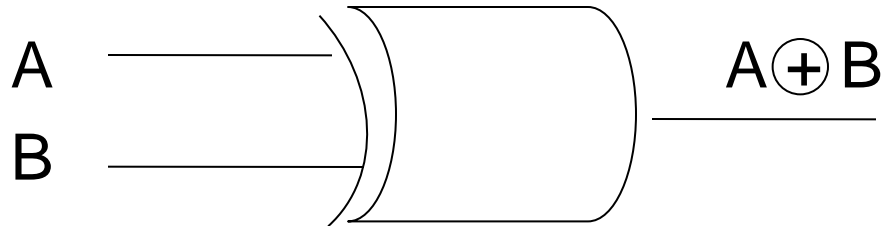

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

The output is 0 if all the inputs are the same

7. The EXCLUSIVE NOR Gate


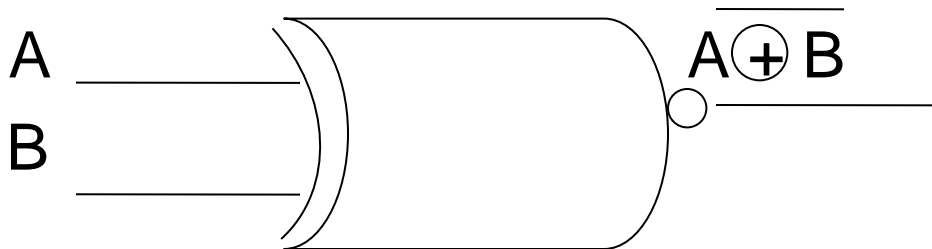


A	B	$\overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1

The output is 1 if all the inputs are the same.

Complex Logic gates

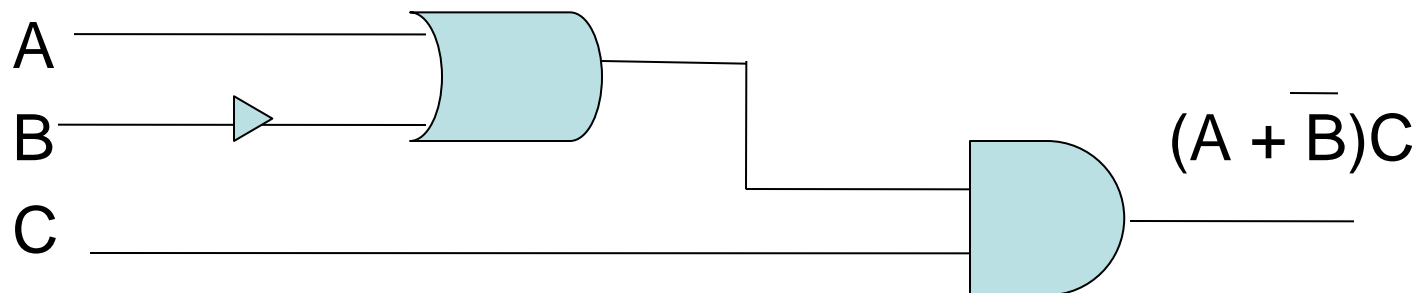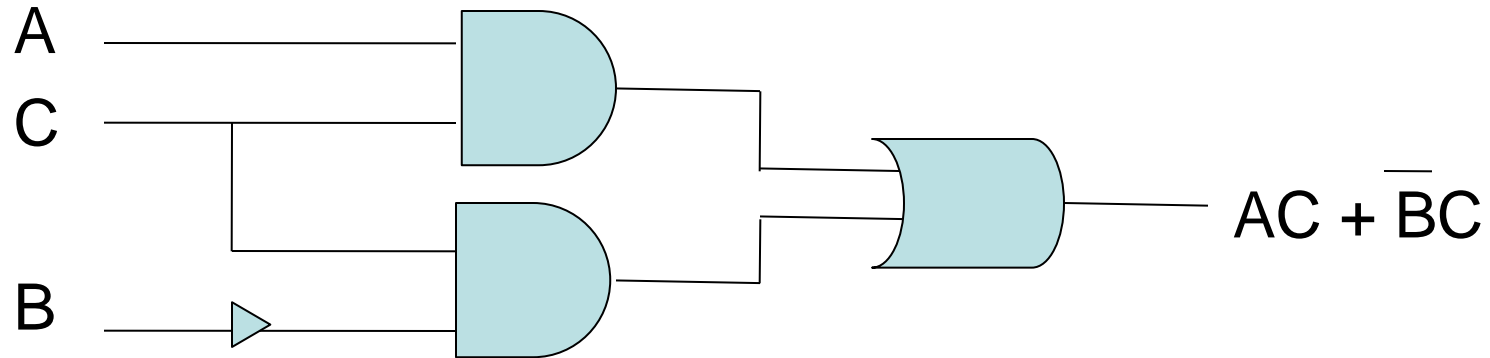- Logic circuits can be built by combining several of the elementary logic gates.
- **A graphical illustration of a logic circuit** is called a **logical diagram**



- Two logic networks that have the same input/output characteristics are said to be **equivalent**.

EXAMPLE

Prove that $AC + \overline{B}C = (A + \overline{B})C$

NOTE:

- The best way to prove equivalence is to use the **truth tables**.

A	B	C	\overline{B}	AC	$\overline{B}C$	$AC + \overline{B}C$	$A + \overline{B}$	$(A + \overline{B})C$
0	0	0	1	0	0	0	1	0
0	0	1	1	0	1	1	1	1
0	1	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0
1	0	0	1	0	0	0	1	0
1	0	1	1	1	1	1	1	1
1	1	0	0	0	0	0	1	0
1	1	1	0	1	0	1	1	1

BOOLEAN ALGEBRA

It is a mathematical structure that consists of a set containing only a 0 and 1, the unary operator (complementation) and the binary operation of addition and multiplication. **Subtraction and Division** are not defined in Boolean algebra

$$A = \overline{\overline{A}}$$

$$AA = A$$

$$A + A = A$$

$$A \cdot 0 = 0$$

$$A + 0 = A$$

$$A \cdot 1 = A$$

$$A + 1 = 1$$

$$A \cdot \overline{A} = 0$$

$$A + \overline{A} = 1$$

$$AB = BA$$

$$A + B = B + A$$

$$(AB)C = A(BC)$$

$$A + (B + C) = (A + B) + C$$

$$A(B + C) = AB + AC$$

$$(B + C)A = BA + CA$$

$$\overline{A + B} = \overline{A} \overline{B}$$

$$\overline{AB} = \overline{A} + \overline{B}$$

$$AB + \overline{A}B = A$$

$$A + \overline{A}B = A$$

$$(A + \overline{B})B = AB$$

$$(A + B)(\overline{A} + \overline{B}) = \overline{A} \overline{B}$$

$$(A + B)(A + C) = A + BC$$

$$A(\overline{A} + B) = \overline{A}B$$

$$AB + \overline{A}B = B$$


$$\overline{AB} + \overline{A}B = \overline{A} \oplus B$$

$$\overline{AB}(A + B) = \overline{A} \oplus B$$

Why Boolean Algebra?

- Its used to simplify logic expressions without changing its functionality.
- Used to prove equivalence of logic networks.

Example 1: Simplify the circuit below using Boolean Algebra.

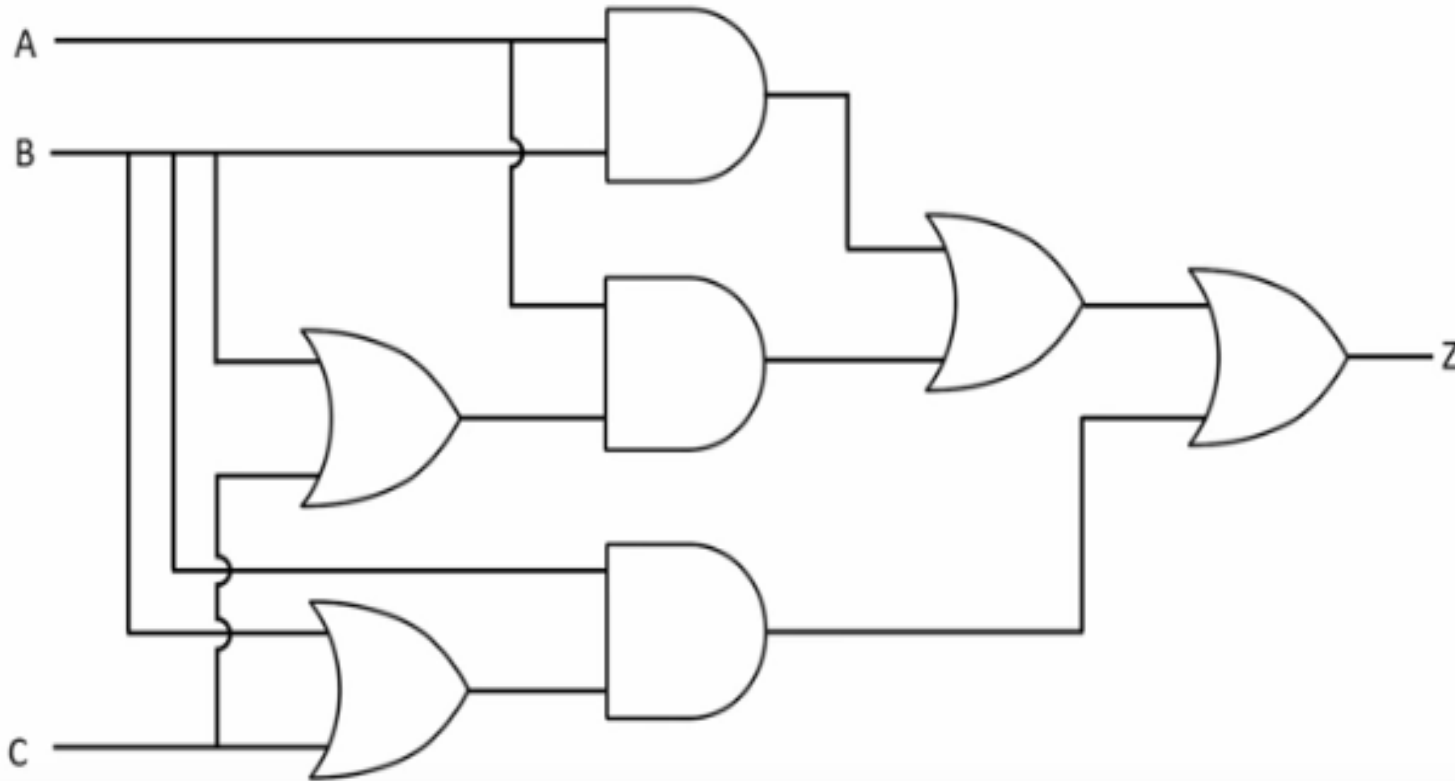

Example 2:

$$\overline{\overline{A}}\overline{\overline{B}}C + BC + AB$$

$$= C(\overline{\overline{A}}\overline{\overline{B}} + B) + AB$$

$$= C(\overline{A} + B) + AB$$

$$= \overline{A}C + BC + AB$$

$$= \overline{A}C + (\overline{A} + A)BC + AB$$

$$= \overline{A}C + \overline{A}BC + ABC + AB$$

$$= \overline{A}C(1 + B) + AB(C + 1)$$

$$= \overline{A}C + AB$$

Prove that $\overline{A}BC + \overline{A}\overline{B}C + A\overline{B}\overline{C} + ABC$ is equivalent to $BC + AC + AB$.

Digital Design Process

- Determine all the input/output relationships that must be true for the network being designed and put them in convenient tabular form.
- Use the drawn up table to find Boolean expressions for each output.
- Simplify the expressions from 2 above
- Use the expressions resulting from step 3 to develop the desired logical diagram.

Three design tools

- Truth Table (*To define a logical network*)
- Boolean Expression (*for minimization*)
- Logic diagram (*For the actual design*)

Example

Design a three input network that will output a 1 if the majority of the inputs are 1's otherwise the output is zero

Step 1 (Draw a truth Table)

A	B	C	X	
0	0	0	0	X_0
0	0	1	0	X_1
0	1	0	0	X_2
0	1	1	1	X_3
1	0	0	0	X_4
1	0	1	1	X_5
1	1	0	1	X_6
1	1	1	1	X_7

Boolean expression

Step 2 (Find the Boolean expression.)

There are two types of Boolean Expressions

1. ***SUM OF PRODUCTS (SOP's)***

We form a product for each row for which the output is 1 and then add the products.

- A product is 1 if and only if all of its factors are 1
- A sum is 1 if at least one of its terms is a 1.

$$X_3 = \bar{A}BC; \quad X_5 = A\bar{B}C; \quad X_6 = ABC\bar{C}; \quad X_7 = ABC$$

$$X = X_3 + X_5 + X_6 + X_7$$

$$X = \bar{A}BC + A\bar{B}C + ABC\bar{C} + ABC$$

Boolean expression

2. *PRODUCT OF SUMS (POS)*

A sum is formed for each row for which the output is zero then the sums are multiplied.

- A sum is 0 if all its terms are 0's.
- A product is 0 if at least one of its factors is 0.

$$X_0 = A + B + C; \quad X_1 = A + B + \bar{C}; \quad X_2 = A + \bar{B} + C; \quad X_4 = \bar{A} + B + C$$


$$X = X_0 X_1 X_2 X_4 = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)(\bar{A} + B + C)$$

Step 3 Simplify the expression

$$\overline{A}BC + A\overline{B}C + A\overline{B}\overline{C} + ABC = BC + AC + AB$$

Digital Design Process

- **Step 4: Draw the logic diagram**

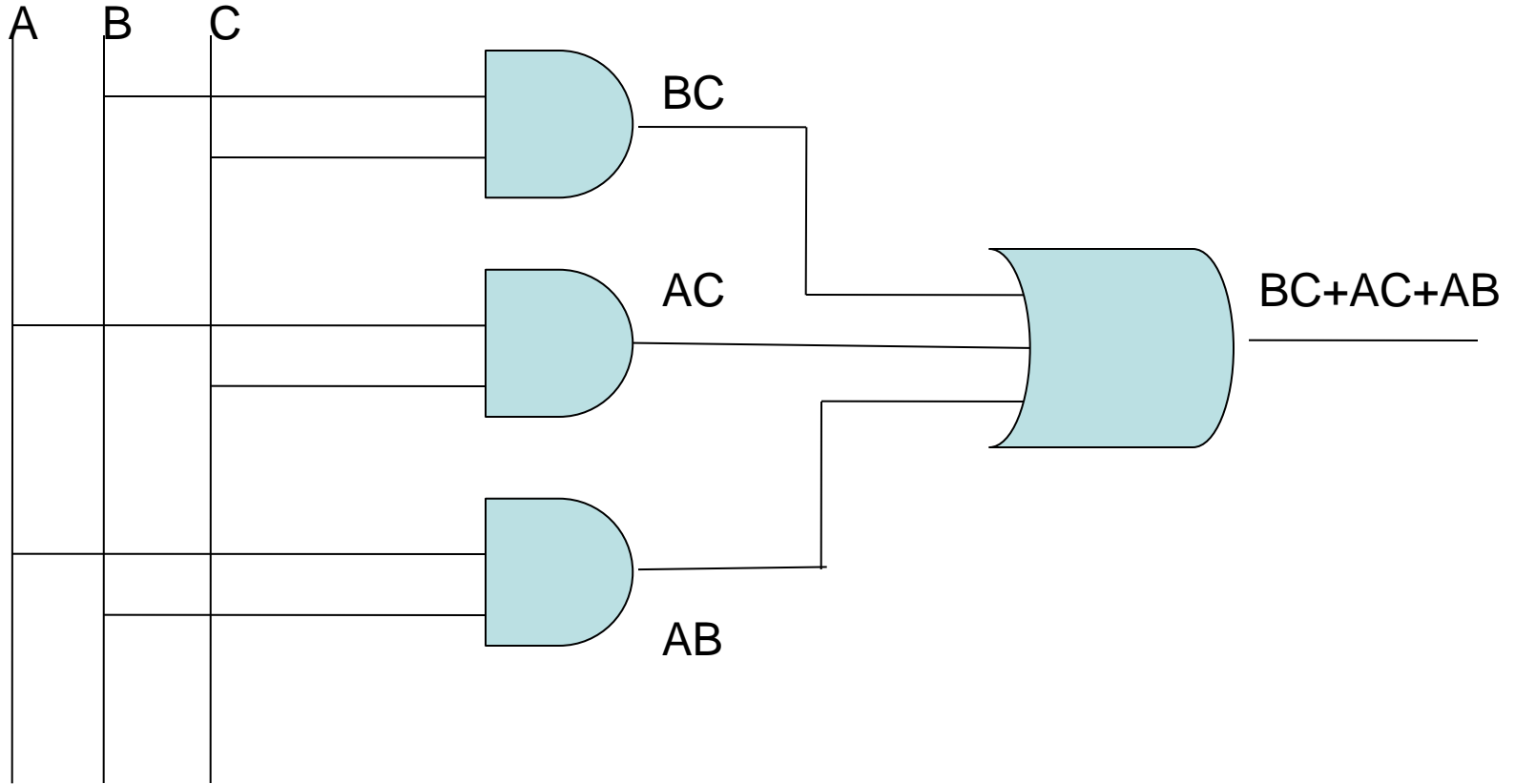

MAXITERMS & MINITERMS

- The occurrence of a variable or its complement in an expression is called a **literal**.
- A term in the SUM OF PRODUCTS that includes a literal for every input is called a **miniterm**.
- A term in the PRODUCT OF SUMS that includes a literal for every input is called a **maxiterm**.
- e.g. in $\bar{A}\bar{B}C + \bar{A}BC + A\bar{C}$; $\bar{A}\bar{B}C$ and $\bar{A}BC$ are miniterms, $A\bar{C}$ is not a miniterm.
- Similarly in $(\bar{A} + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + C)$, $(\bar{A} + B + \bar{C})$ and $(A + \bar{B} + \bar{C})$ are maxiterms, $(\bar{A} + C)$ is not.

KARNAUGH MAPS

- A Karnaugh map is a truth table for a single output consisting of arrays of squares where each square corresponds to a row of a truth table. It is used in simplifying Boolean algebra expressions.
- The symbols at the top represent the variables associated with the columns and the symbols on the left represent the variables associated with the rows.
- The value of each output for each input is put in the corresponding square.
- For each 1 in the Karnaugh map there is a corresponding miniterm in the output's Sum of product expression and each 0 represents a maxiterm in the Product of Sums expression.

EXAMPLES

Two inputs

		A	
		0	1
B	0	0	2
	1	1	3

Three Inputs

		AB			
		00	01	11	10
C	0	0	2	6	4
	1	1	3	7	5

Four Inputs

		AB			
		00	01	11	10
CD	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

Rules of Grouping in K-maps

- 1) A group must only contain 1s no 0s.
- 2) A group can only be horizontal or vertical not diagonal.
- 3) A group must contain 2^n 1s i.e 1,2,4,8.
- 4) Each group should be as large as possible.
- 5) Groups may overlap
- 6) Groups may wrap around a table.
- 7) Every 1 must be in at least one group.
- 8) There should be as few groups as possible.

EXAMPLE 1

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Using Boolean Algebra

$$X = \overline{A}BC + A\overline{B}\overline{C} + ABC$$

$$= \overline{A}BC + ABC + A\overline{B}\overline{C} + ABC$$

$$= BC + AB$$

Look for adjacent groups that include 2^n miniterms where n is an integer. The larger the group the greater is the reduction.

		AB			
		00	01	11	10
C	0	0	0	1	0
	1	0	1	1	0

EXAMPLE 2


A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Using Boolean simplification:

$$\overline{A}BC + \overline{A}B\overline{C} + A\overline{B}C + ABC$$

$$\overline{A}BC + ABC + \overline{A}B\overline{C} + A\overline{B}C \quad \overline{A}B\overline{C} + ABC$$
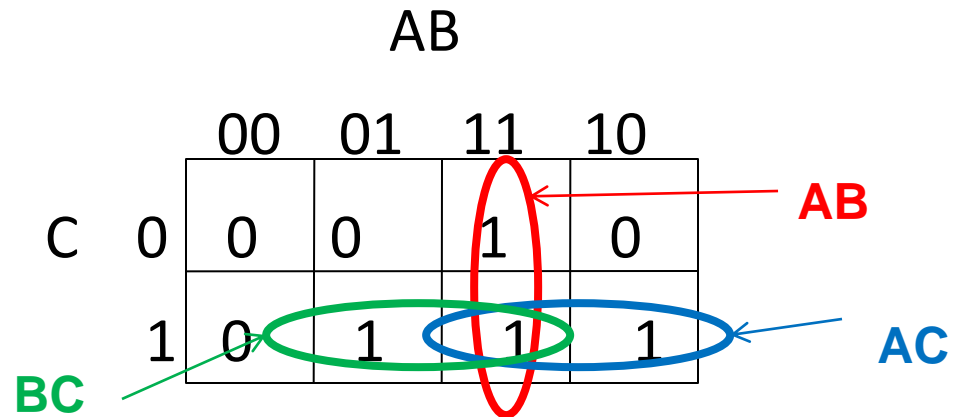
$$= \mathbf{BC} + \mathbf{AC} + \mathbf{AB}$$



A function may be used to state where the output is 1 instead of drawing a Karnaugh map. e.g. for the above example

$$F(A,B,C) = \Sigma(3,5,6,7)$$



EXAMPLE 3

$$F(A,B,C) = \Sigma(0,1,2,3,7)$$



		AB			
		00	01	11	10
C	0	1	1		
	1	1	1	1	

A red rectangle highlights the cells (0,0), (0,1), (1,0), and (1,1). A red arrow points from the label \bar{A} to the boundary between the first and second columns. A blue oval highlights the cells (1,0), (1,1), (1,2), and (1,3). A blue arrow points from the label BC to the boundary between the third and fourth columns.

More Examples

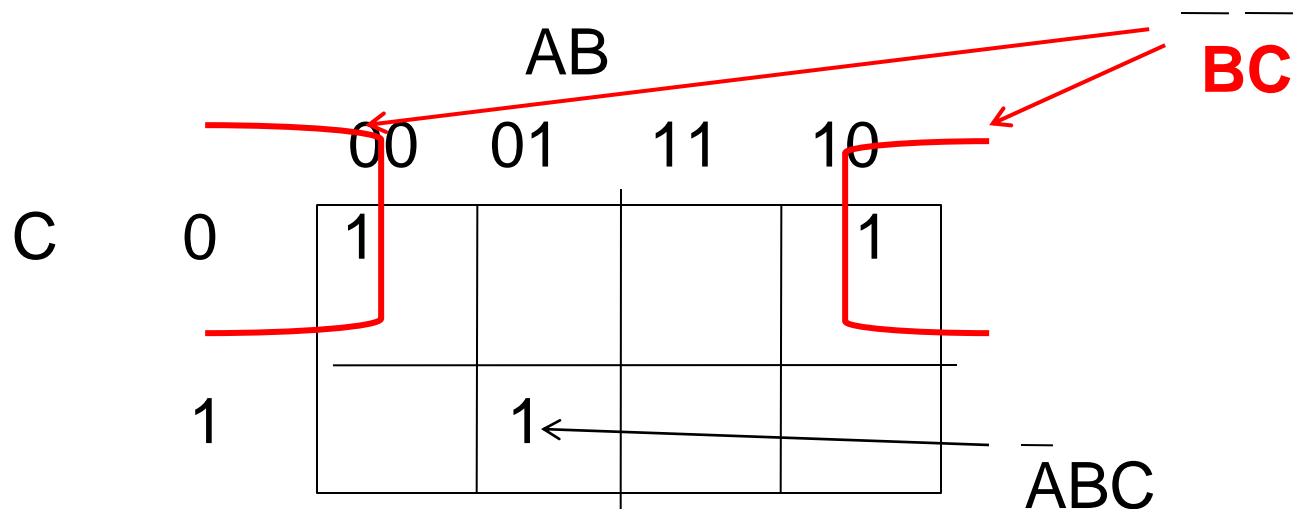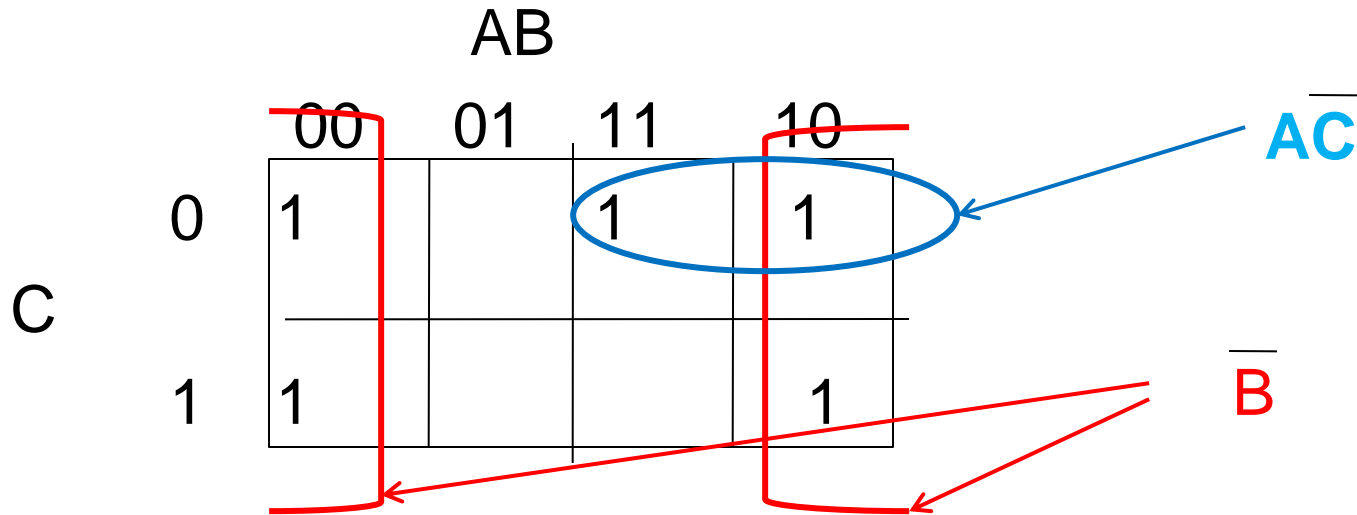


More Examples

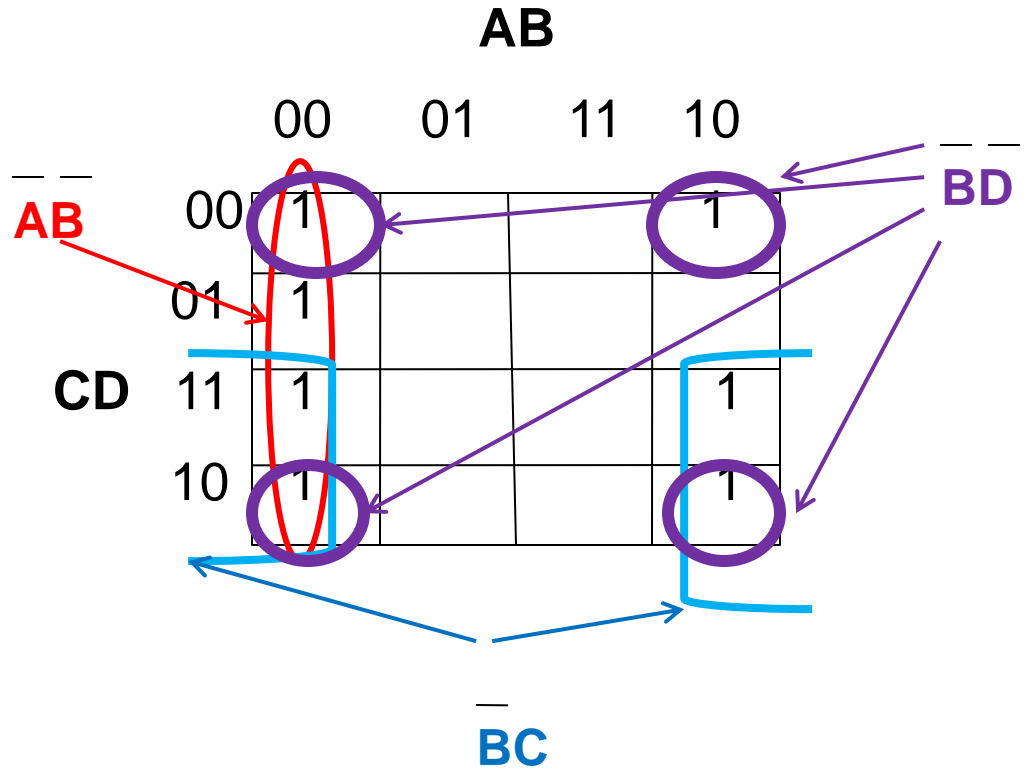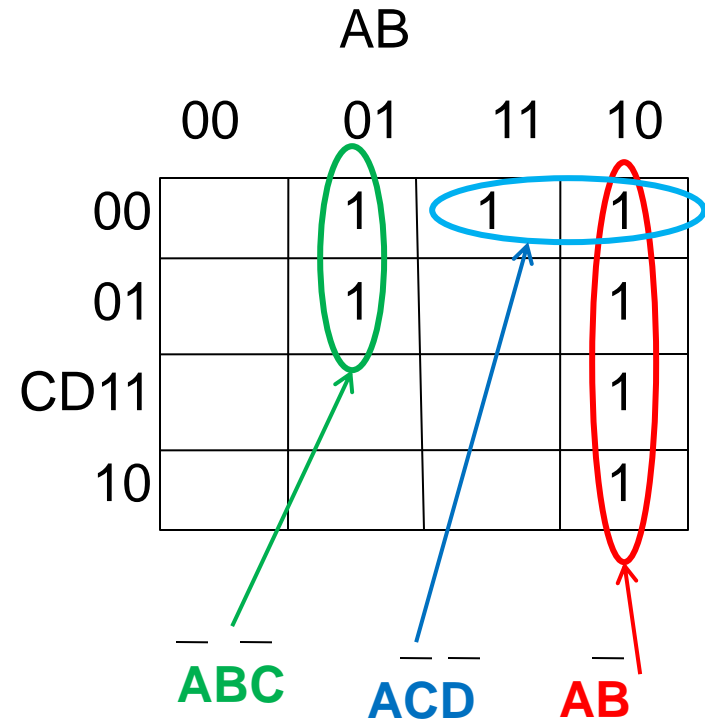

THE DON'T CARE CASES

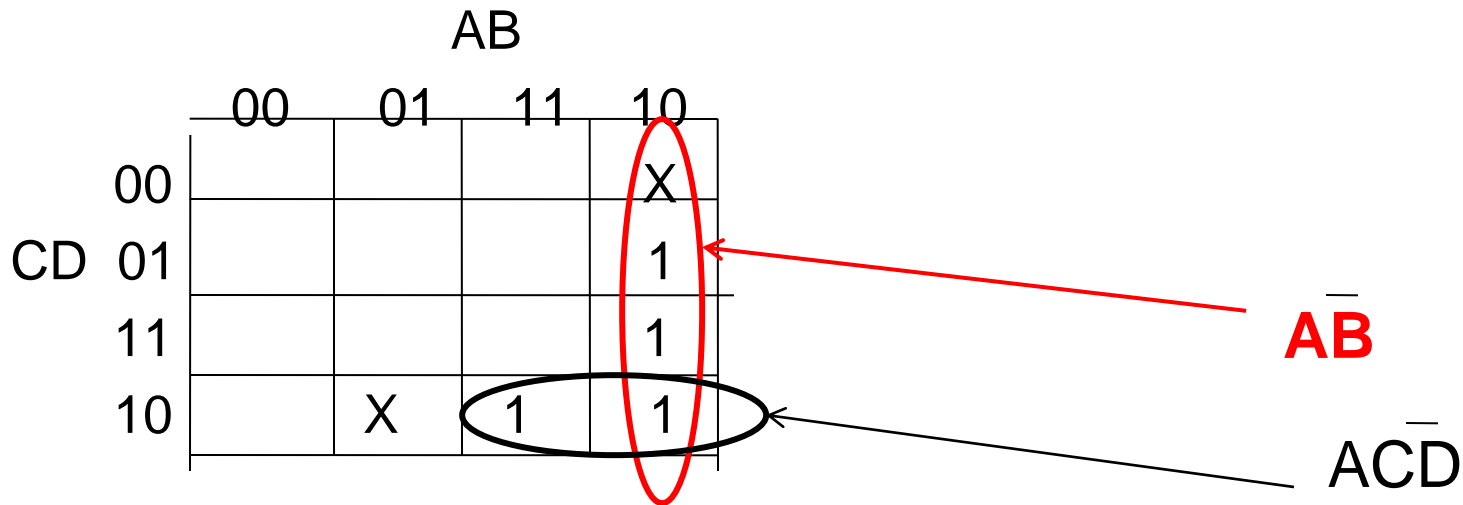- For some designs some input combinations cannot occur. Their outputs are represented by X's in the Karnaugh Map and they may or may not be included in the prime implicants.
- They are called **Don't Care Cases** denoted by the function $d(A,B,C) = \Sigma(\dots)$



In the example above it is important to include the miniterm $\bar{A}\bar{B}\bar{C}\bar{D}$ in but not $\bar{A}\bar{B}C\bar{D}$

Reading Assignment 4:

- Read more about The Don't care cases as used in Karnaugh maps.