

# CHAPTER 4

## COMBINATORIAL CIRCUITS

# COMBINATORIAL CIRCUITS

In this chapter we look at the different combinatorial circuits;


1. Adders
2. Multiplexer and Demultiplexers
3. Comparators
4. Decoders and Encoders
5. ROMs and PLAs.

# ADDERS

- An adder is a digital circuit in electronics that implements addition of binary numbers.
- Adders are of 3 types:
  - Half Adder
  - Full Adder
  - Ripple carry Adder

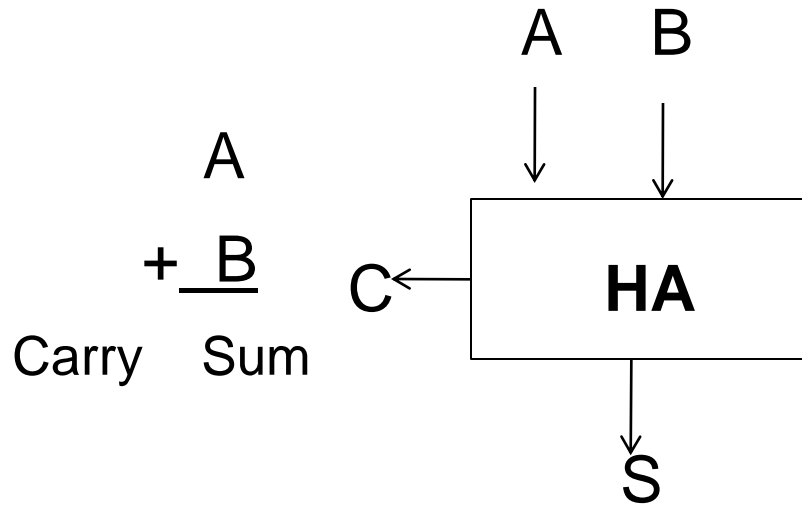
# HALF ADDER

It is a circuit for adding 2, 1 bit quantities.



$$C = AB$$
$$S = \bar{A}B + A\bar{B} = A \oplus B$$


A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

# Example: Adding 2 binary numbers.

Now let's try a binary addition  $1011 + 0011 = 1110$      $11 + 3 = 14$


Carry in	0	1	1	0
Digit 1	1	0	1	1
Digit 2	0	0	1	1
Sum	1	1	1	0
Carry Out	0	0	1	1



We have to keep carrying through so we need multiple adders, each with 3 inputs
 
# Full Adder

It is an adder that includes a carry input from a lower order sum.




$$\begin{aligned}C_o &= \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC \\&= C(\bar{A}B + A\bar{B}) + AB(\bar{C} + C) \\&= \mathbf{C(A \oplus B) + AB}\end{aligned}$$

$$\begin{aligned}S &= \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \\&= \bar{A}(\bar{B}\bar{C} + B\bar{C}) + A(\bar{B}\bar{C} + BC)\end{aligned}$$

A	B	C <sub>i</sub>	S	C <sub>o</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned}&= \bar{A}(B \oplus C) + A(\overline{B \oplus C}) \\&= \mathbf{A \oplus B \oplus C}\end{aligned}$$

# FULL ADDER

 

# Ripple Carry Adder


It is a circuit built up of many full adders consisting of the required number of bits.

**The carry out bit is used as a carry in into its left neighbour.** The carry into the right most bit is set to 0.




# Ripple Carry Adder

8 bit adder

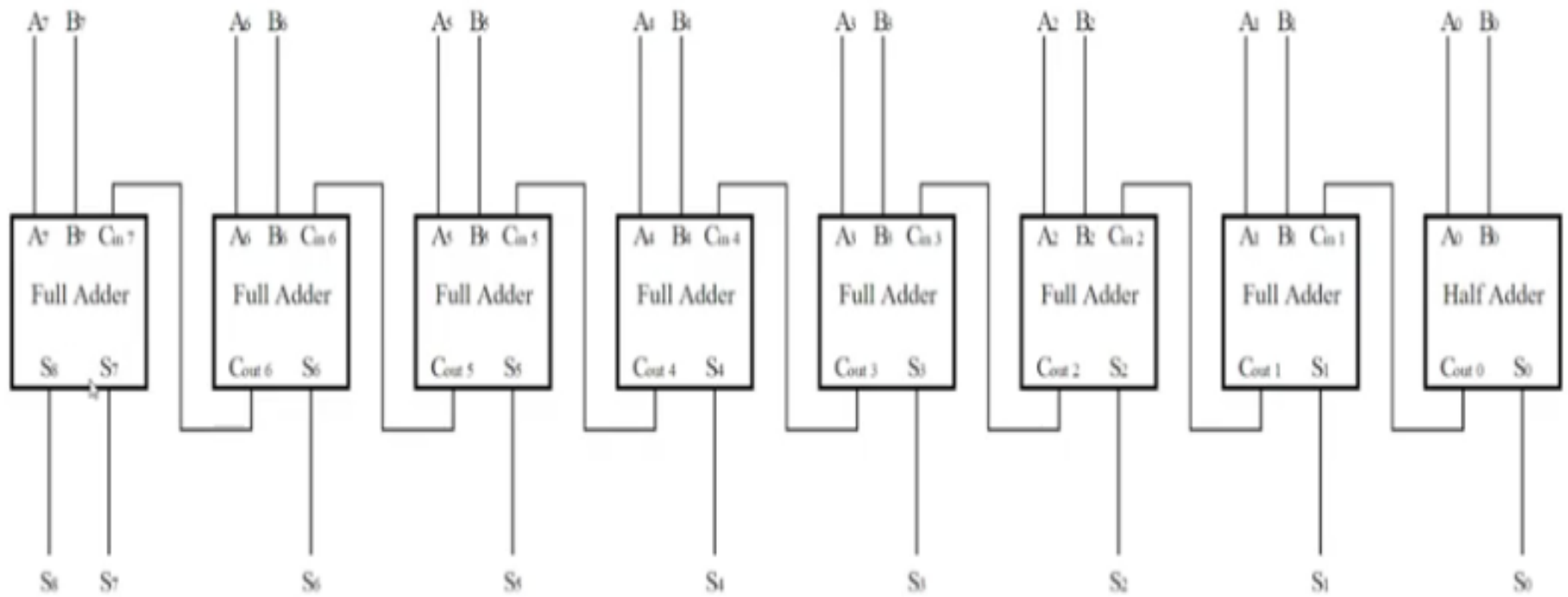
 
# A Multiplexer (Data Selector)

- It is a logical network capable of selecting a single set of data inputs from a number of sets of inputs and it passes the selected inputs to the outputs.
- A multiplexer has 2 kinds of inputs, the **control inputs** and the **data inputs**.
- The control inputs are used to select which of the inputs in the data is to be passed through to the outputs.




## 2-1 Multiplexer

It has 2 data inputs A and B, one control input , P, and one output, X.  
When the control input  $P = 0$  the output X is A and when  $P = 1$   $X = B$


P	A	B	X
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1
 
$$\begin{aligned}X &= \bar{P}A\bar{B} + \bar{P}AB + P\bar{A}\bar{B} + PAB \\&= \bar{P}A(\bar{B} + B) + PB(\bar{A} + A) \\&= \bar{P}A + PB\end{aligned}$$


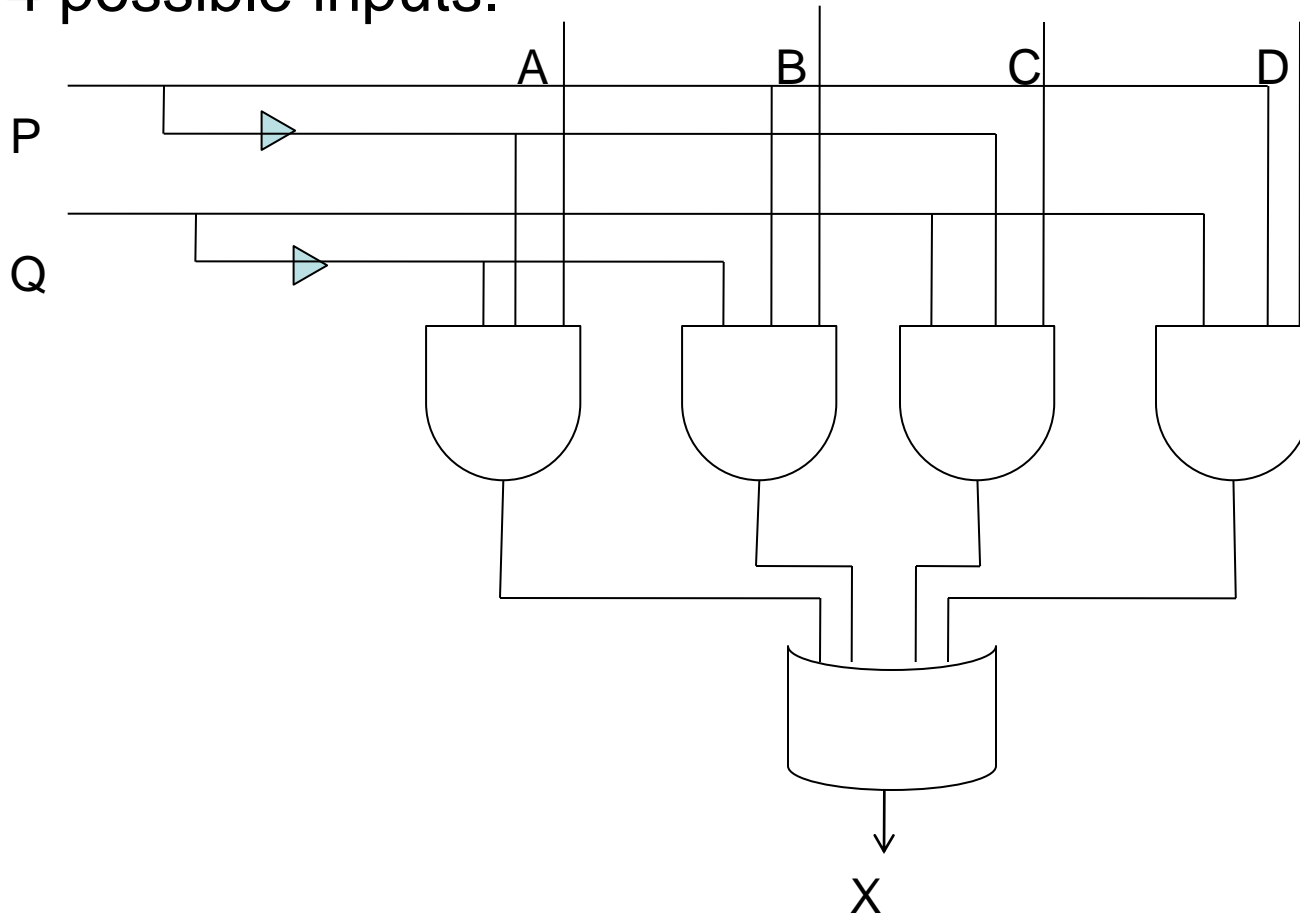
# 4-1 Multiplexer


It selects only one of the 4 inputs. It has 2 control lines to choose one of the 4 possible inputs.



In general for an **n to 1** multiplexer, the inequality  **$2^k = n$**  must be satisfied where  **$k = \text{number of control lines}$** .

 
# A Demultiplexer

It has 1 set of data inputs and two or more sets of outputs and a set of control inputs whose purpose is to select the set of outputs to transmit. The other outputs are 0.


 
# A 1- 2 Demultiplexer


It has 1 data input (A) , two outputs( X, Y) and one control input (P) .



P	A	X	Y
0	0	0	0
0	1	1	0
1	0	0	0
1	1	0	1

$$X = \bar{P}A;$$


$$Y = PA$$

 
 
# Comparators

A comparator compares two sets of inputs and outputs a 1 if the comparison is satisfied.

The comparisons are  $=$ ,  $\neq$ ,  $>$ ,  $\geq$ ,  $<$ ,  $\leq$




For equality comparator, the design is based upon the XNOR gate which outputs a 1 if its inputs are the same and a 0 if they are not equal.

# 1 bit > comparator

The output is 1 if  $A > B$

$$X = A\bar{B}$$

A	B	X
0	0	0
0	1	0
1	0	1
1	1	0

 



# Decoder


Circuit **whose outputs are minterms of the inputs**. Exactly only one output is a 1 at any given time.

If **n** is the number of inputs and **m** the number of outputs then  $2^n \geq m$

e.g. if the binary number on the input lines is **k** then output line **k** will be 1 and all the others will be 0's.

<b>A<sub>1</sub></b>	<b>A<sub>2</sub></b>	<b>A<sub>3</sub></b>	<b>X<sub>0</sub></b>	<b>X<sub>1</sub></b>	<b>X<sub>2</sub></b>	<b>X<sub>3</sub></b>	<b>X<sub>4</sub></b>	<b>X<sub>5</sub></b>	<b>X<sub>6</sub></b>	<b>X<sub>7</sub></b>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

# Decoder

 

# The Encoder

The opposite of a decoder. Only one input can be a 1 (activated) at a time. Its number in binary is presented as the output.

It has  $2^n$  inputs and  $n$  outputs.

$A_0$	$A_1$	$A_2$	$A_3$	$X_1$	$X_2$
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

Inputs					Outputs		
$A_1$	$A_2$	$A_3$	$A_4$	$A_5$	$X_1$	$X_2$	$X_3$
1	0	0	0	0	0	0	1
0	1	0	0	0	0	1	0
0	0	1	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	0	0	1	1	0	1

$$X_3 = A_1 + A_3 + A_5$$

$$X_2 = A_2 + A_3$$


$$X_1 = A_4 + A_5$$

# Encoder

$$X_3 = A_1 + A_3 + A_5$$

$$X_2 = A_2 + A_3$$

$$X_1 = A_4 + A_5$$

 


# Code Converters

They are electronic circuits whose purpose is to convert data from one format to another.

Data in a computer system may take on several different forms as it changes from one format to another.

e.g. the decimal input from a keyboard calculator must be converted into BCD using an encoder.

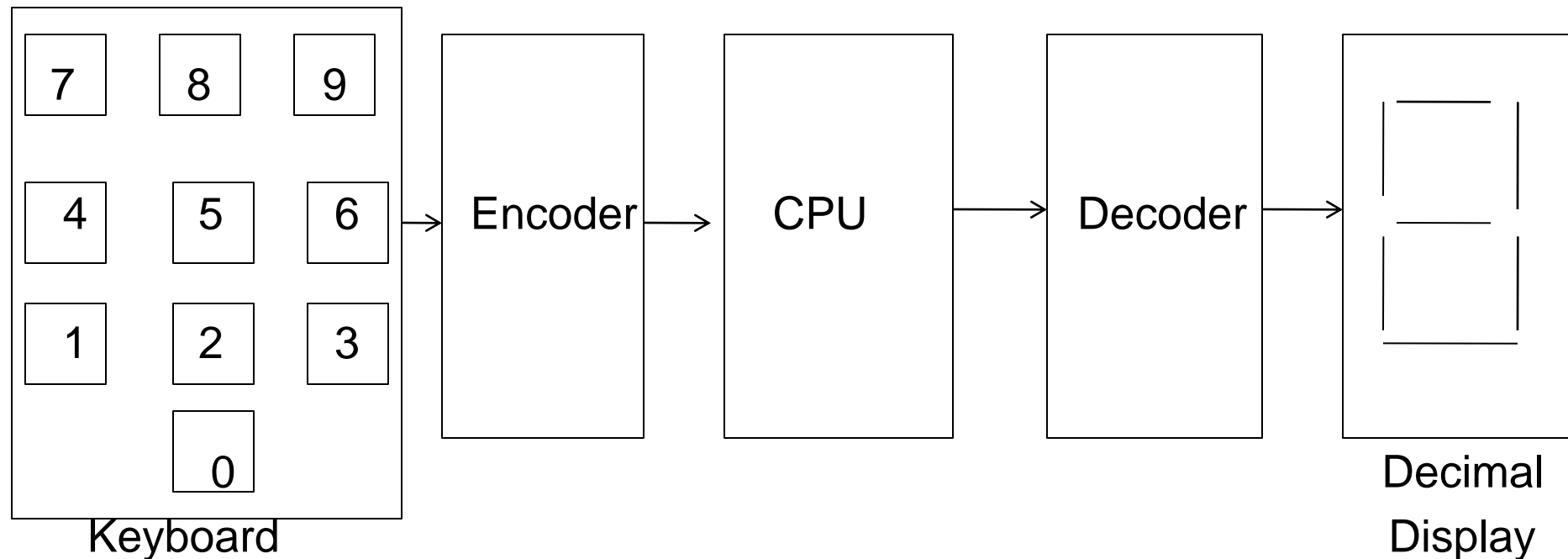
The CPU's output is in BCD and the decoder translates the BCD to a special 7 segment display code.



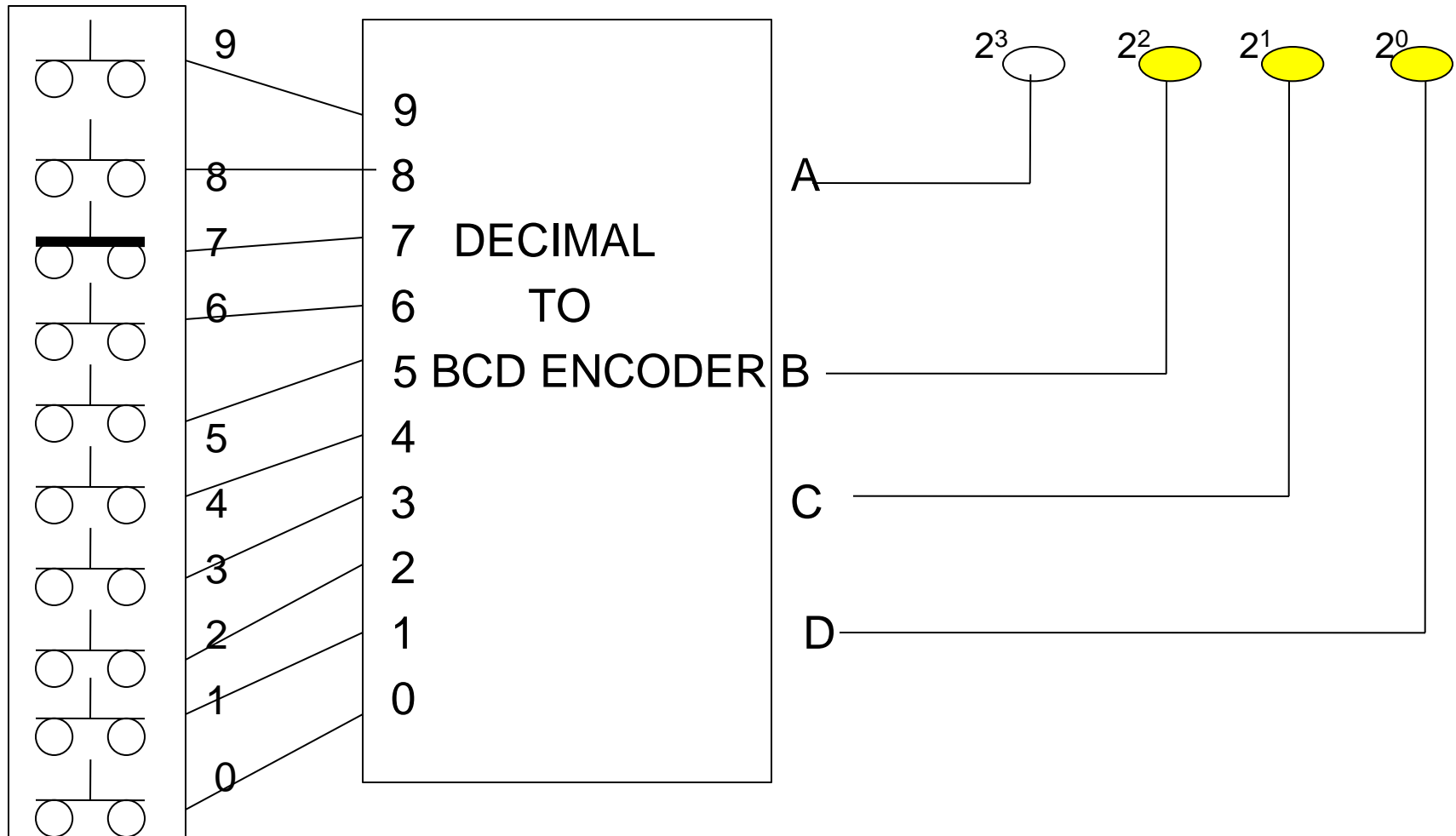
# The encoder circuit

The encoder has 10 active inputs and 4 outputs connected to input lamps.


e.g. The input 7 causes a BCD output of 0111.



# The Decoder circuit

 

# The Display

 

A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	0	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1



# ROMS AND PLA'S

## ROM (Read Only Memory)

- Its circuit is equivalent to a decoder. It outputs all possible minterms of the inputs followed by an encoder.
- The output combinations are permanently embedded in its circuitry and the inputs serve to select one of these combinations. Each output is obtained by disconnecting the OR inputs from the AND gates whose minterms are not to be included in the output.
- Because a ROM must produce all the possible minterms its decoder portion is fixed by  $n$  (the number of inputs). The encoder portion depends on both the outputs and the way in which all the outputs of a decoder are used to generate the final ROM outputs.

# ROMS




Once the disconnections are made they cannot be changed.  
(ROM nature)

## EXAMPLE

Construct a 2 input ( A,B) and 3 output (X,Y,Z) ROM such that:

$$X = A\bar{B} + AB; \quad Y = \bar{A}B + A\bar{B}; \quad Z = \bar{A}B + AB$$

# ROM EXAMPLE

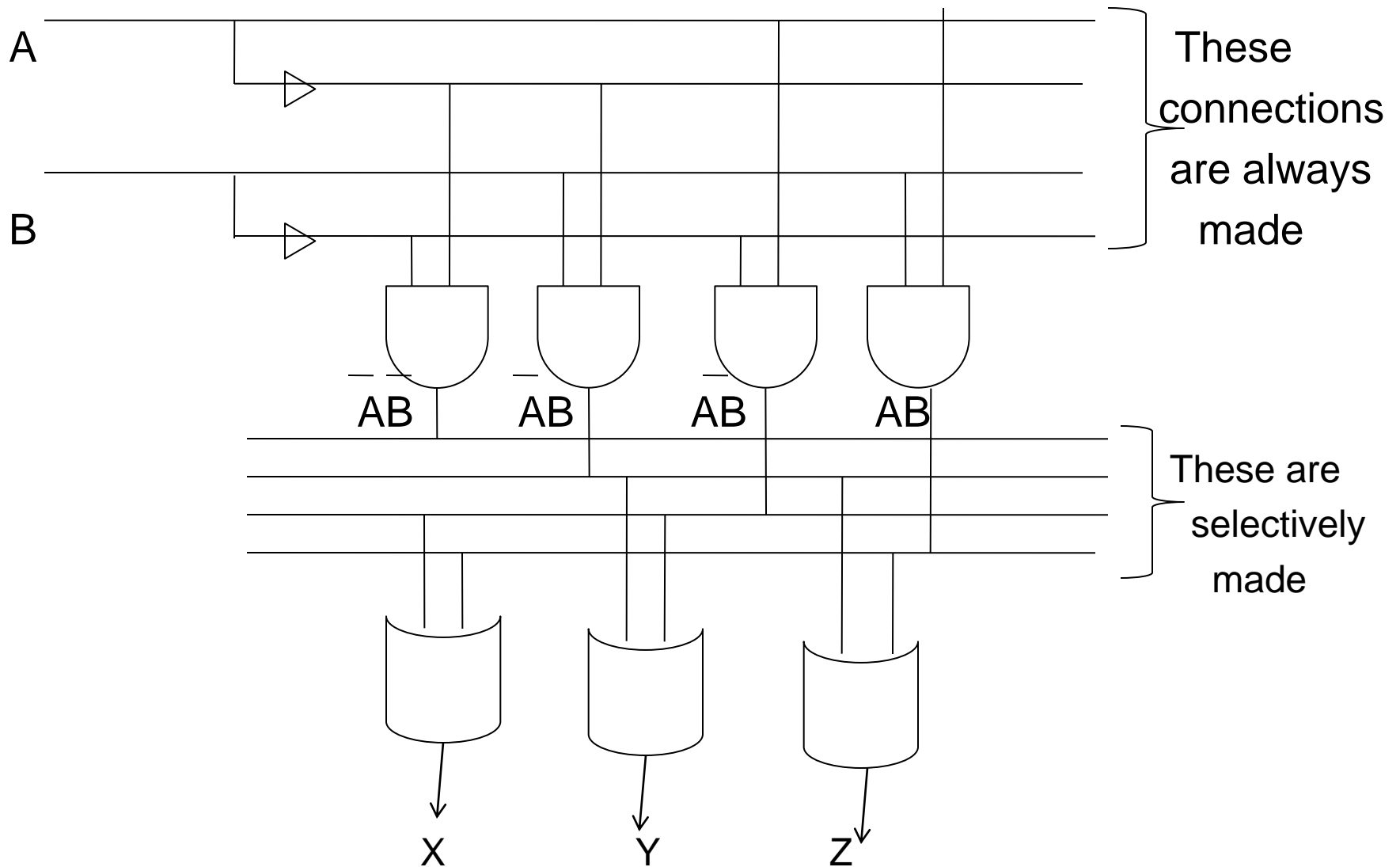

# PLA (Programmed Logic Array)


- Similar to a ROM but does not output miniterms that will not be needed in any of the outputs. i.e. the decoder does not necessarily produce all the miniterms. For an  $n$  input network, we have  $\leq 2^n$  AND gates



## EXAMPLE

Implementation of the above ROM as a PLA

# PLA example

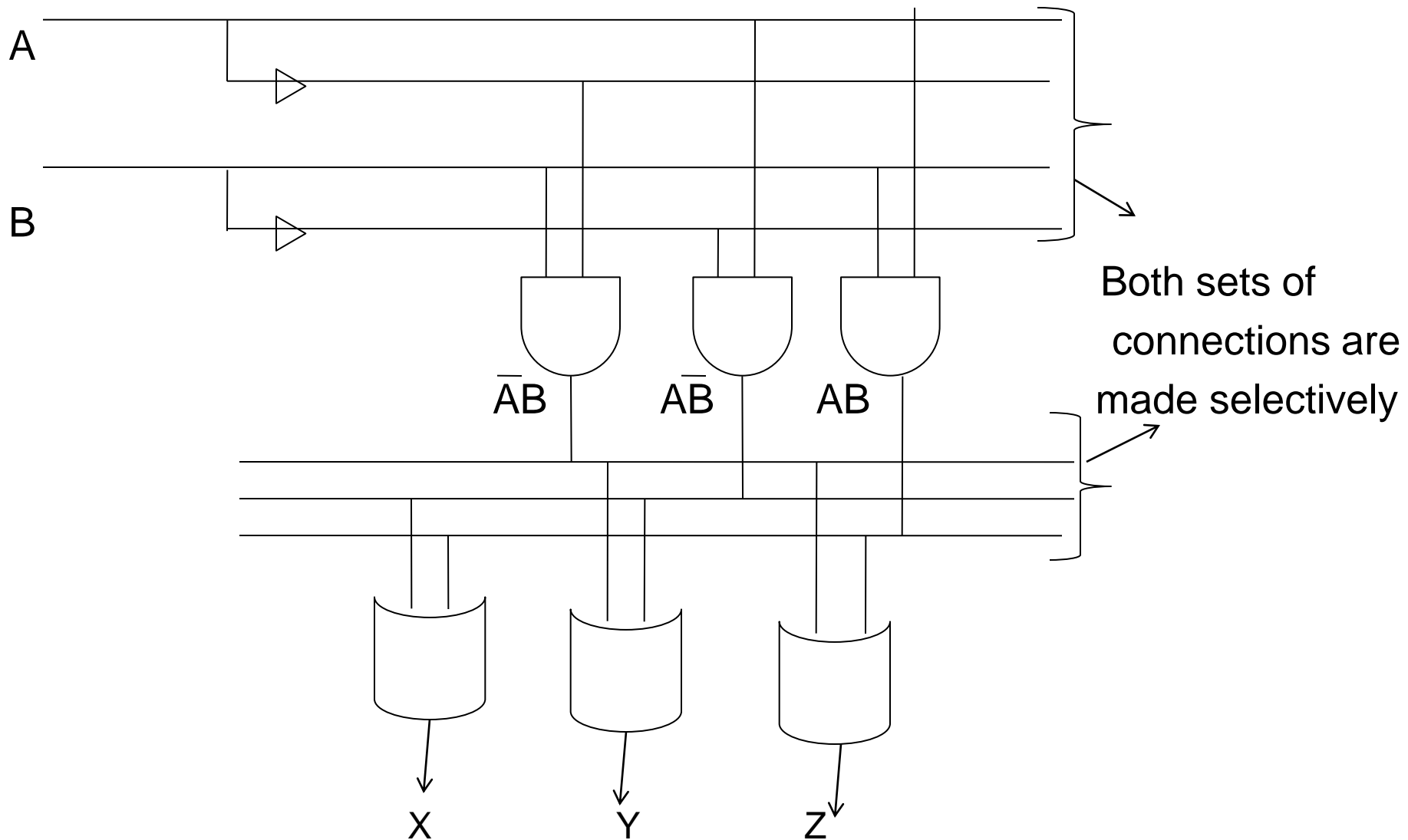

# Reading Assignment 4

1. Read and make notes on the following circuits:

- a) Half Subtractor
- b) Full Subtractor

Note:

- Examine the 4 steps you go through to design the circuit.